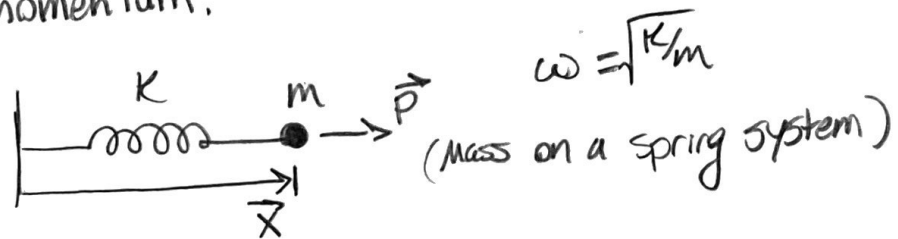


The LC Tank Oscillator

Before, in my "Quantum Harmonic Oscillator Derivation" Notes, we investigated a harmonic oscillator based on a mechanical system with well-defined position and momentum.



We wrote down a Hamiltonian

$$H = \frac{\hat{p}^2}{2m} + \frac{1}{2} m \omega^2 \hat{x}^2$$

Applied the First Quantization with

$$\begin{cases} \hat{x} = x \\ \hat{p} = -i\hbar \frac{\partial}{\partial x} \end{cases}$$


Eventually, we wrote down the second quantization of the QHO Hamiltonian as

$$H = \hbar\omega \left(\frac{1}{2} + a^\dagger a \right)$$


Unfortunately, this is not enough to make a qubit. We can't make a qubit with a mass & spring system since #1) A Harmonic Oscillator is a bad qubit, we need an anharmonic oscillator and #2) We don't have any quantum ingredients... quantum technology cannot be built by only classical ingredients; we need at least one quantum ingredient.

Luckily for us, we can meet both criteria #1 and #2 in the superconducting circuit world. The LC Tank circuit is the electrical analog of a mass on a spring system

Mechanical
Harmonic
Oscillator

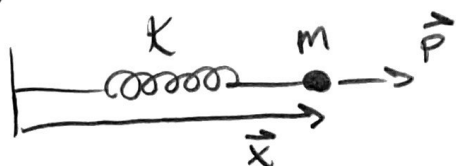
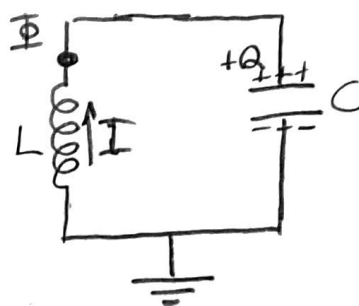
$$H = \frac{\hat{p}^2}{2m} + \frac{1}{2} m \omega^2 \hat{x}^2$$



Electrical
Harmonic
Oscillator.

$$H = \underbrace{\frac{1}{2} C V^2}_{\text{Energy of a capacitor}} + \underbrace{\frac{1}{2} L I^2}_{\text{Energy of an inductor}}$$

$$H = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$$

Where Q is the charge on a capacitor plate; $Q = CV$

And Φ is the Flux through an inductor; $\Phi = LI$

It's more appropriate to express $H = \frac{Q^2}{2C} + \frac{\Phi^2}{2L}$ in terms of superconducting circuit language.

We define:

- Reduced Flux: $\phi \equiv 2\pi \Phi / \Phi_0$; $\Phi_0 = \frac{h}{2e}$ "Magnetic Flux Quantum"

- Reduced Charge: $n \equiv \frac{Q}{2e}$ (Excess number of Cooper pairs on the island)

- Charging Energy: $E_C \equiv \frac{e^2}{2C}$ (Energy required to add a Cooper pair to the island)

- Inductive Energy: $E_L = \frac{(\Phi_0/2\pi)^2}{L}$ (Proportional to the energy of an inductor)

Utilizing these definitions, we can derive

$$H = 4E_C n^2 + \frac{1}{2} E_L \phi^2$$

Proof: Show that $\mathcal{H} = \frac{Q^2}{2C} + \frac{\Phi^2}{2L} = 4E_C n^2 + \frac{1}{2} E_L \phi^2$

$$\mathcal{H} = 4E_C n^2 + \frac{1}{2} E_L \phi^2$$

$$\mathcal{H} = 4 \left(\frac{e^2}{2C} \right) \left(\frac{Q}{e} \right)^2 + \frac{1}{2} \left[\left(\frac{\Phi_0 / 2\pi}{L} \right)^2 \right] \left(\frac{2\pi \Phi}{\Phi_0} \right)^2$$

$$\mathcal{H} = 4 \left(\frac{e^2}{2C} \right) \left(\frac{Q^2}{e^2} \right) + \frac{1}{2} \left(\frac{\Phi_0^2}{4\pi^2 L} \right) \left(\frac{4\pi^2 \Phi^2}{\Phi_0^2} \right)$$

$$\mathcal{H} = \frac{Q^2}{2C} + \frac{1}{2} \frac{\Phi^2}{L}$$

Let's compare the mechanical - electrical Hamiltonian analogs

$$\mathcal{H} = \frac{p^2}{2m} + \frac{1}{2} m \omega^2 x^2 \quad (\text{Mechanical})$$

$$\mathcal{H} = \frac{Q^2}{2C} + \frac{\Phi^2}{2L} \quad (\text{Electrical})$$


$$= 4E_C n^2 + \frac{1}{2} E_L \phi^2 \quad (\text{Superconducting Circuit})$$

Here, the analog between the mechanical & electrical variables seems to be

	Electrical		Mechanical	
charge	Q	\longleftrightarrow	p	momentum
flux	Φ	\longleftrightarrow	x	position
capacitance	C	\longleftrightarrow	m	mass
Inductance	L	\longleftrightarrow	$\frac{1}{m\omega^2} = \frac{1}{k}$	Inverse Spring Constant

Things to do: • write a and a^\dagger in terms of electrical variables
• Make a note that $[\hat{\Phi}, \hat{Q}] = i\hbar$

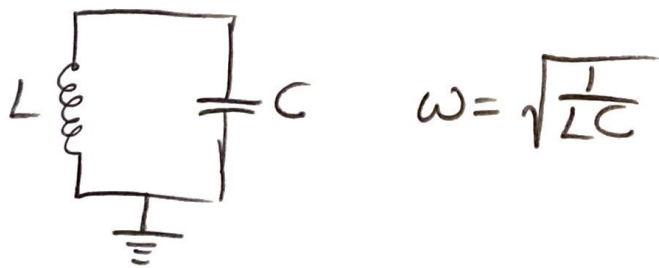The resonant frequency of an LC circuit is



$\omega = \frac{1}{\sqrt{LC}}$ is written in terms of electrical circuit language.

To translate to superconducting circuit language we should write L and C in terms of E_L and E_C , respectively.

$$E_C = \frac{e^2}{2C} \quad E_L = \frac{(\Phi_0/2\pi)^2}{L}$$

$$C = \frac{e^2}{2E_C} \quad L = \frac{(\Phi_0/2\pi)^2}{E_L}$$

$$LC = \left(\frac{e^2}{2E_C} \right) \left(\frac{1}{E_L} \left(\frac{\Phi_0}{2\pi} \right)^2 \right)$$

$$LC = \left(\frac{e^2}{2E_C} \right) \left(\frac{\Phi_0^2}{4\pi^2 E_L} \right)$$

$$LC = \frac{e^2 \Phi_0^2}{8\pi^2 E_C E_L}$$

$$\omega^2 = \frac{1}{LC} = \frac{\pi^2}{e^2 \Phi_0^2} E_C E_L$$

$$\omega = \frac{\pi}{e \Phi_0} \sqrt{E_C E_L}$$

Substituting in $\Phi_0 = \frac{h}{2e}$

$$\omega = \frac{\pi}{e} \cdot \frac{2e}{h} \sqrt{E_C E_L}$$

$$\boxed{\omega = \sqrt{8E_C E_L} / \hbar}$$

Resonant Frequency of the LC circuit in terms of charging and inductance energies.